

# DTEL

(Department for Technology Enhanced Learning)  
The Centre for Technology enabled Teaching & Learning , N Y S S, India



Teaching Innovation - Entrepreneurial - Global

**DEPARTMENT OF COMPUTER  
TECHNOLOGY  
IV-SEMESTER  
COMPUTER ARCHITECTURE AND  
ORGANIZATION  
  
UNIT NO.4  
ARITHMETICS**

# UNIT 4:- SYLLABUS

- 1 Number Representation , Addition of Positive numbers
- 2 Logic Design for fast adders
- 3 Addition and Subtraction , Arithmetic and Branching conditions
- 4 Multiplications of positive numbers, Signed-Operand multiplication
- 5 Fast Multiplication, Booth's Algorithm
- 6 Integer Division, Floating point numbers and operations

The student will be able to:



**Design of Arithmetic unit to perform fixed point**

**and floating point arithmetic operations.**

# LECTURE 1: ARITHMETICS


## Add of signed & unsigned nos

$x_i$	$y_i$	Carry-in $c_i$	Sum $s_i$	Carry-out $c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i = \bar{x}_i \bar{y}_i c_i + \bar{x}_i y_i \bar{c}_i + x_i \bar{y}_i \bar{c}_i + x_i y_i c_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = y_i c_i + x_i c_i + x_i y_i$$

Example:

 

At the  $i^{th}$  stage:

Input:


$c_i$  is the carry-in

Output:

$s_i$  is the sum

$c_{i+1}$  carry-out


to  $(i+1)^{st}$  state

 

Full Adder (FA): Symbol for the complete circuit for a single stage of addition.

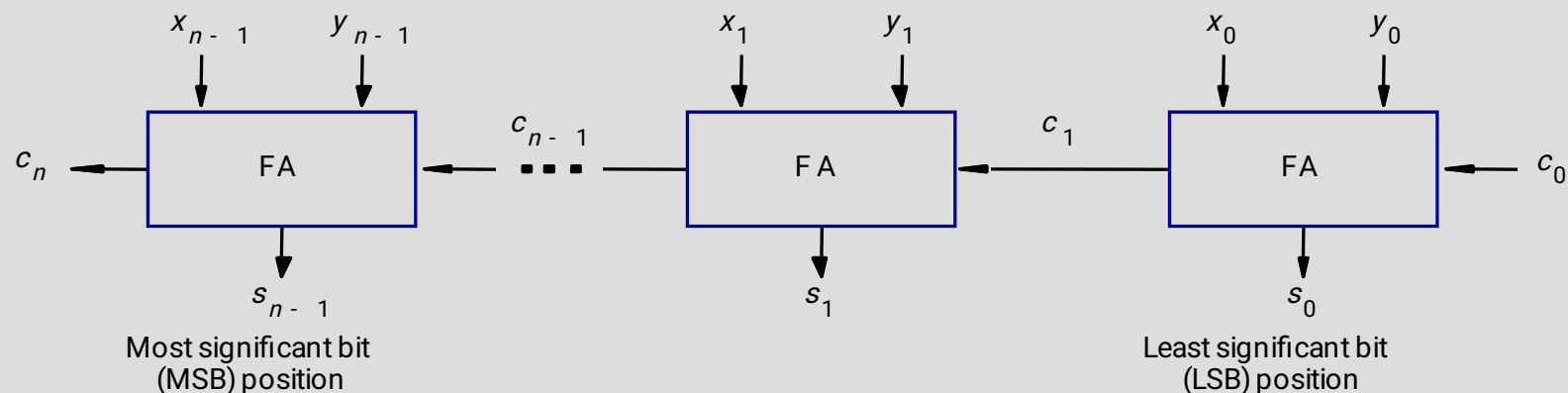
## Adder

- Cascade  $n$  full adder (FA) blocks to form a  $n$ -bit adder.
- Carries propagate or ripple through this cascade,  $n$ -bit ripple carry adder.



Carry-in  $c_0$  into the LSB position provides a convenient way to perform subtraction.

 
$K$   $n$ -bit numbers can be added by cascading  $k$   $n$ -bit adders.



Each  $n$ -bit adder forms a block, so this is cascading of blocks. Carries ripple or propagate through blocks, Blocked Ripple Carry Adder




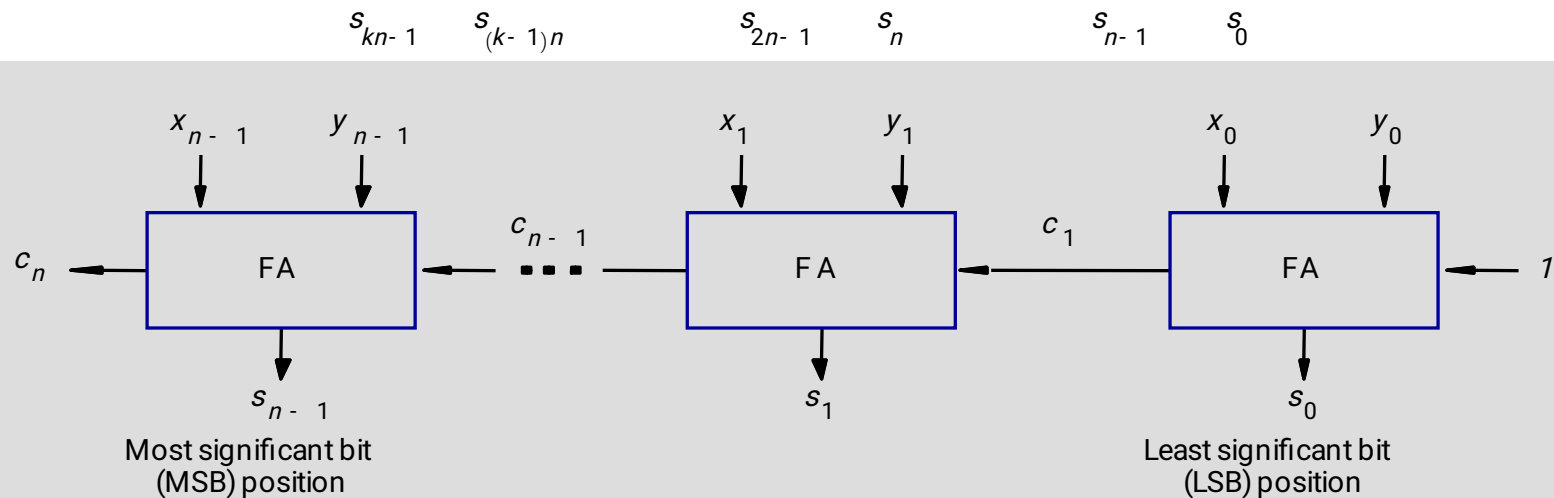- Recall  $X - Y$  is equivalent to adding 2's complement of  $Y$  to  $X$ .
- 2's complement is equivalent to 1's complement + 1.
- $X - Y = X + Y + 1$
- 2's complement of positive and negative numbers is computed similarly.



# LECTURE 1: ARITHMETICS


## n-bit adder/subtractor (contd)

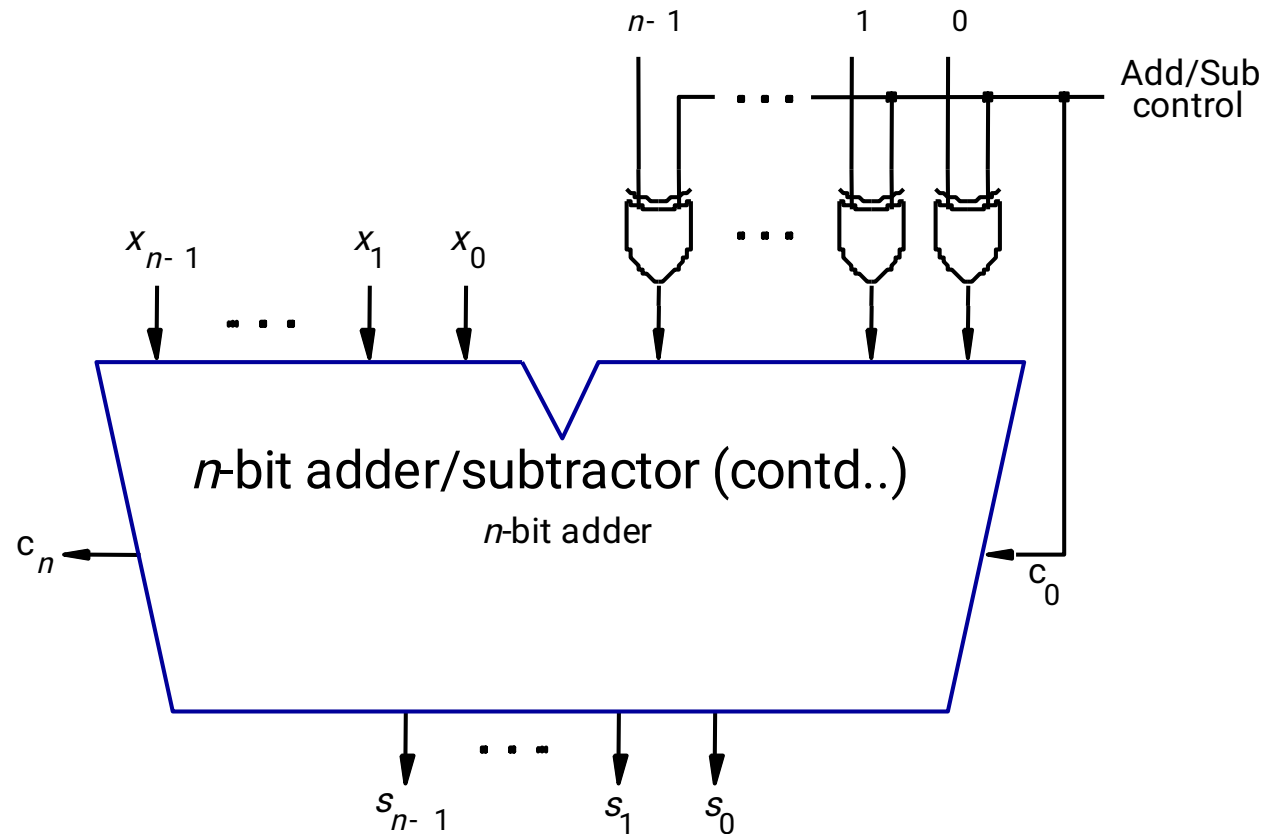



- Add/sub control = 0, addition.
- Add/sub control = 1, subtraction.

- Overflows can only occur when the sign of the two operands is the same.
- Overflow occurs if the sign of the result is different from the sign of the operands.
- Recall that the MSB represents the sign.
  - $x_{n-1}, y_{n-1}, s_{n-1}$  represent the sign of operand  $x$ , operand  $y$  and result  $s$  respectively
- Circuit to detect overflow. can be implemented by the following logic expressions:


Consider  $0^{th}$  stage:

 

  - $c_1$  is available after 2 gate delays.
- $s_1$  is available after 1 gate delay.


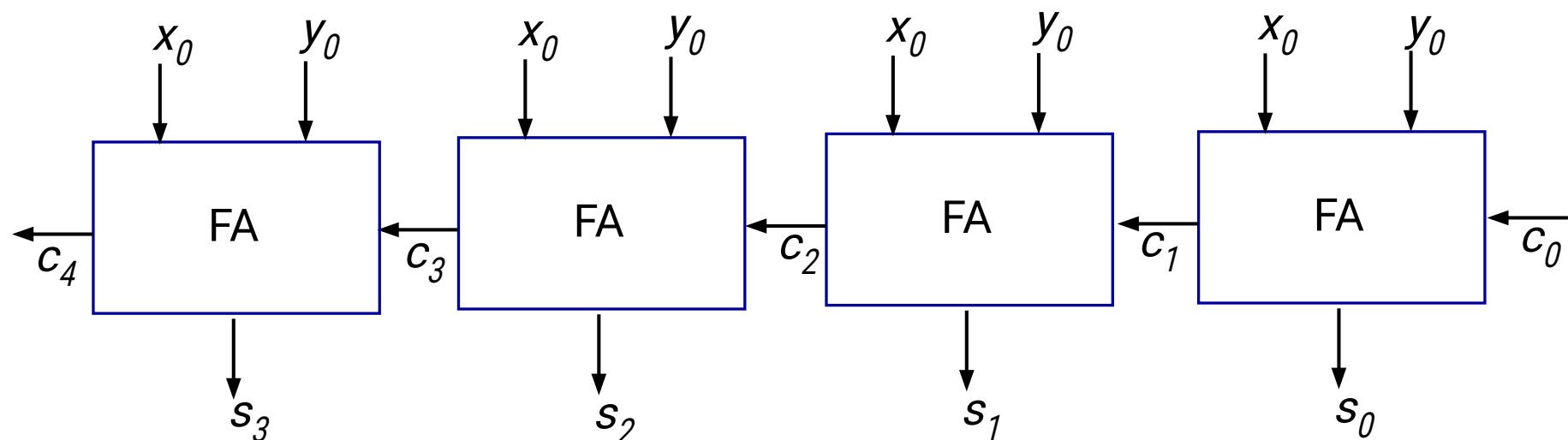
## Cascade of 4 Full Adders, or a 4-bit adder



- $s_0$  available after 1 gate delays,  $c_1$  available after 2 gate delays.
- $s_1$  available after 3 gate delays,  $c_2$  available after 4 gate delays.
- $s_2$  available after 5 gate delays,  $c_3$  available after 6 gate delays.
- $s_3$  available after 7 gate delays,  $c_4$  available after 8 gate delays.

For an  $n$ -bit adder,  $s_{n-1}$  is available after  $2n-1$  gate delays  
 $c_n$  is available after  $2n$  gate delays

Recall the equations:

Addition

$$s_i = x_i \oplus y_i \oplus c_i$$

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

Second equation can be written as:  $c_{i+1} = x_i y_i + (x_i + y_i) c_i$

We can write:  $c_{i+1} = G_i + P_i c_i$   
where  $G_i = x_i y_i$  and  $P_i = x_i + y_i$

- $G_i$  is called generate function and  $P_i$  is called propagate function
- $G_i$  and  $P_i$  are computed only from  $x_i$  and  $y_i$  and not  $c_i$ , thus they can be computed in one gate delay after  $X$  and  $Y$  are applied to the inputs of an  $n$ -bit adder.

$$c_{i+1} = G_i + P_i c_i$$

$$c_i = G_{i-1} + P_{i-1} c_{i-1}$$

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} c_{i-1})$$

*continuing*

$$\Rightarrow c_{i+1} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} c_{i-2}))$$

*until*

$$c_{i+1} = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_1 G_0 + P_i P_{i-1} \dots P_0 c_0$$

- All carries can be obtained 3 gate delays after  $X$ ,  $Y$  and  $c_0$  are applied.
  - One gate delay for  $P_i$  and  $G_i$
  - Two gate delays in the AND-OR circuit for  $c_{i+1}$ .
- This is called Carry Lookahead adder.

- Performing  $n$ -bit addition in 4 gate delays independent of  $n$  is good only theoretically because of fan-in constraints.
- Last AND gate and OR gate require a fan-in of  $(n+1)$  for a  $n$ -bit adder.
- In order to add operands longer than 4 bits, we can cascade 4-bit Carry-Lookahead adders. Cascade of Carry-Lookahead adders is called Blocked Carry-Lookahead adder.



$$c_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 c_0$$

Rewrite this as:

$$P_0' = P_3 P_2 P_1 P_0$$

$$G_0' = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0$$


*Subscript I denotes the blocked carry lookahead and identifies the block.*

Cascade 4 4-bit adders,  $c_{16}$  can be expressed as:

$$c_{16} = G_3' + P_3' G_2' + P_3' P_2' G_1' + P_3' P_2' P_1^0 G_0' + P_3' P_2' P_1^0 P_0^0 c_0$$

# LECTURE 1:- ARITHMETICS

## Blocked carry lookahead Adder

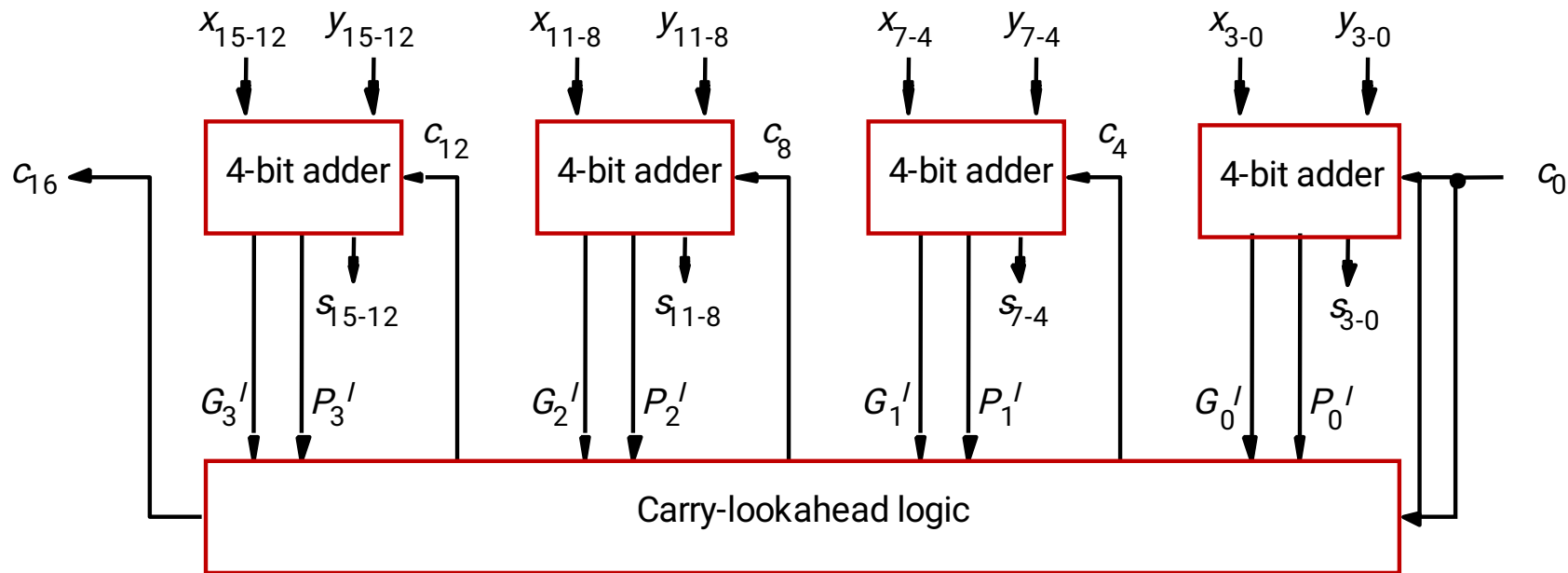

After  $x_i, y_i$  and  $c_0$  are applied as inputs:

- $G_i$  and  $P_i$  for each stage are available after 1 gate delay.
- All carries are available after 5 gate delays.
- $c_{16}$  is available after 5 gate delays.

②

$$C_i = A_i \oplus B_i \oplus C_{in}$$

$$C_{i+1} = P_i C_i + G_i$$

$$P_i = A_i \oplus B_i$$

$$G_i = A_i \cdot B_i$$

put  $i=0$ . 2<sup>nd</sup> Full adder

$$C_{i+1} = P_i C_i + G_i$$

$$C_1 = P_0 C_0 + G_0$$

$$= (A_0 \oplus B_0) C_0 + A_0 \cdot B_0$$

put  $i=1$  (3<sup>rd</sup> F.A)

$$C_2 = P_1 C_1 + G_1$$

$$= P_1 (P_0 C_0 + G_0) + G_1$$

$$C_2 = P_1 P_0 C_0 + P_1 G_0 + G_1$$

put  $i=2$  (4<sup>th</sup> F.A)

$$C_3 = P_2 C_2 + G_2$$

$$= P_2 (P_1 P_0 C_0 + P_1 G_0 + G_1) + G_2$$

$$C_3 = P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2$$

put  $i=3$  For  $C_4$

$$C_4 = P_3 C_3 + G_3$$

$$= P_3 (P_2 P_1 P_0 C_0 + P_2 P_1 G_0 + P_2 G_1 + G_2) + G_3$$

$$C_4 = P_3 P_2 P_1 P_0 C_0 + P_3 P_2 P_1 G_0 + P_3 P_2 G_1 + P_3 G_2 + G_3$$

$$\begin{aligned} \text{Ex: } A &= \begin{pmatrix} 1 & 1 & 0 & 1 \\ 1 & 0 & 1 & 1 \end{pmatrix} \\ S_0 &= x_0 \oplus y_0 \oplus C_0 \\ &= 1 \oplus 1 \oplus 0 \end{aligned}$$

$$\begin{aligned} &= 0 \\ \boxed{C_{i+1} = G_i + P_i C_i} \text{ put } C=0. \\ C_1 &= G_0 + P_0 C_0 \end{aligned}$$

$$\begin{aligned} &= (A_0 B_0) + (A_0 \oplus B_0) C_0 \\ &= 1 \cdot 1 + 0 \cdot 0 \end{aligned}$$

$$C_1 = 1$$

$$C=1$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \\ &= 0 + 1 \cdot 1 \\ &= 1 \end{aligned}$$

$$C=2$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \\ &= 0 + 1 \cdot 0 + 1 \cdot 1 \cdot 1 \\ &= 1 \end{aligned}$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \\ &= 1 + \\ &= 1 \end{aligned}$$

$$\begin{array}{ccc|c} \text{XOR} & & & \\ 0 & 0 & & \\ 0 & 1 & & \\ 1 & 0 & & \\ 1 & 1 & & 0 \end{array}$$

THANK YOU

# LECTURE 2: ARITHMETICS

## Multiplication of unsigned numbers

				1	1	0	1	(13) Multiplicand M
				1	0	1	1	(11) Multiplier Q
				<hr/>				
				1	1	0	1	
			1	1	0	1		
		0	0	0	0			
	1	1	0	1				
<hr/>								
1	0	0	0	1	1	1	1	(143) Product P


**Product of 2  $n$ -bit numbers is at most a  $2n$ -bit no.**

Unsigned multiplication can be viewed as addition of shifted versions of the multiplicand.

## Multiplication of unsigned numbers Multiplication


- We added the partial products at end.
  - Alternative would be to add the partial products at each stage.
- Rules to implement multiplication are:
  - If the  $i^{th}$  bit of the multiplier is 1, shift the multiplicand and add the shifted multiplicand to the current value of the partial product.
  - Hand over the partial product to the next stage
  - Value of the partial product at the start stage is 0.

## Typical multiplication cell

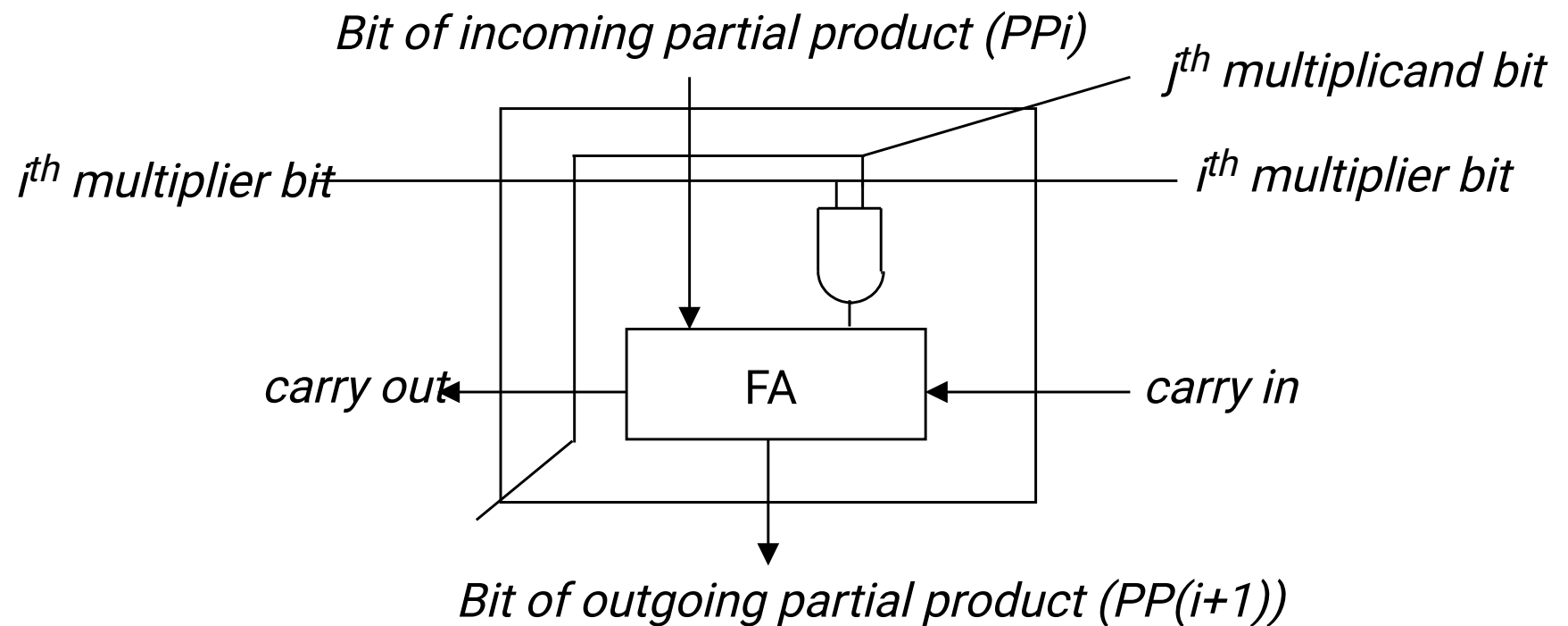



## Combinatorial array multiplier

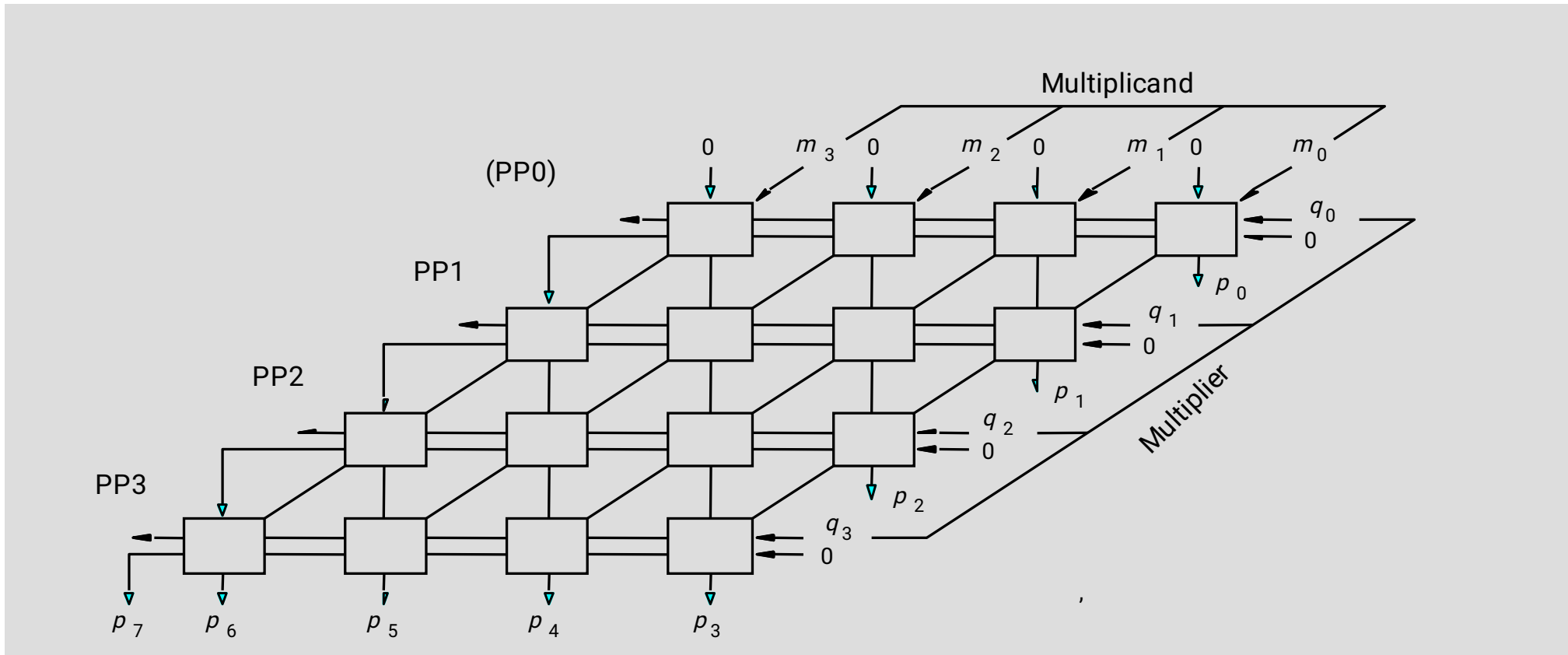

Multiplicand is shifted by displacing it through an array of adders.

### Combinatorial array multiplier


- Combinatorial array multipliers are:
  1. Extremely inefficient.
  2. Have a high gate count for multiplying numbers of practical size such as 32-bit or 64-bit numbers.
  3. Perform only one function, namely, unsigned integer product.
- Improve gate efficiency by using a mixture of combinatorial array techniques and sequential techniques requiring less combinational logic.

### Sequential multiplication

- Recall the rule for generating partial products:
  1. If the  $i$ th bit of the multiplier is 1, add the appropriately shifted multiplicand to the current partial product.
  2. Multiplicand has been shifted left when added to the partial product.
- However, adding a left-shifted multiplicand to an unshifted partial product is equivalent to adding an unshifted multiplicand to a right-shifted partial product

## Sequential Circuit Multiplier


## Multiplication

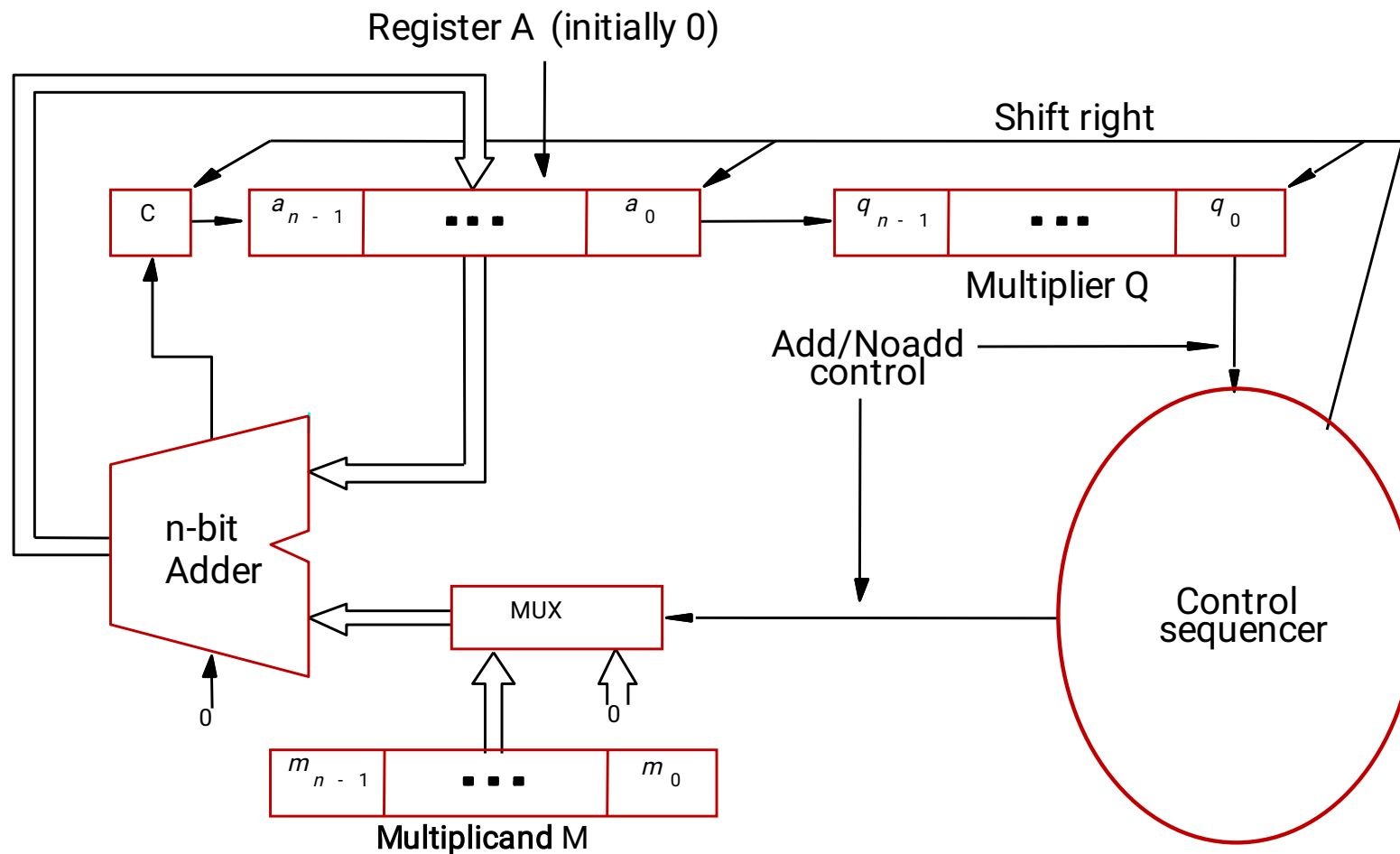


# LECTURE 2: ARITHMETICS
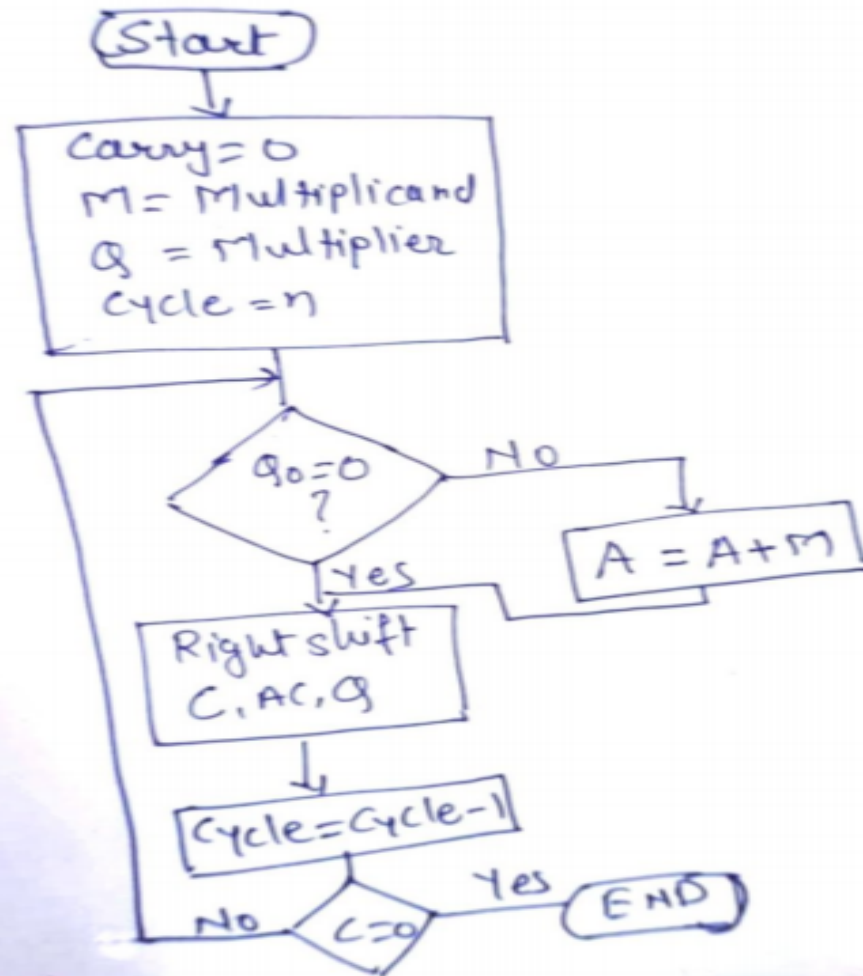
## UNIT-4 CAO

o Algorithm for multiplying fixed point unsigned number



## Sequential multiplication

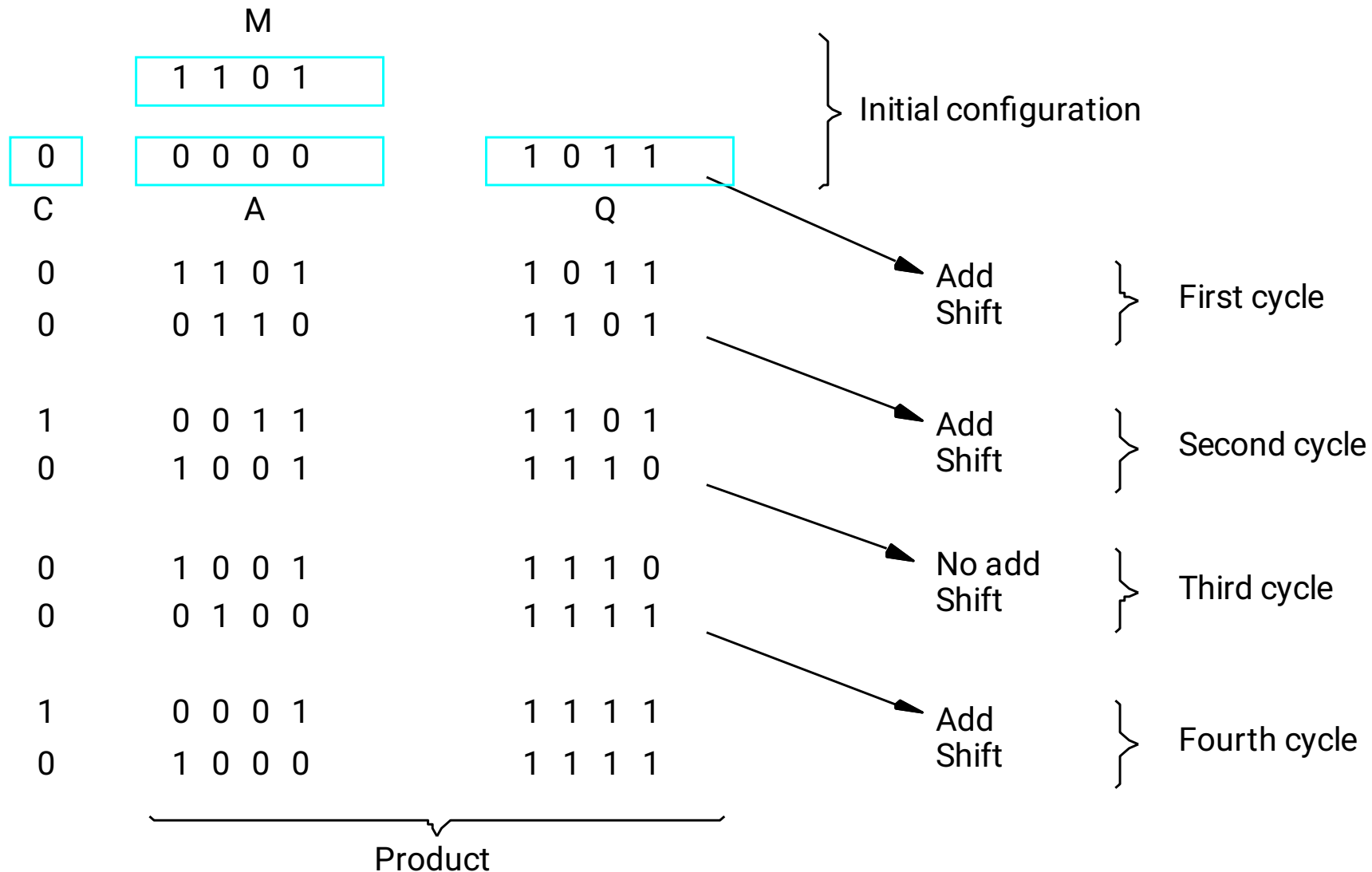

THANK YOU

Multiplier		Version of multiplicand selected by bit
Bit <i>i</i>	Bit <i>i</i> -1	
0	0	0XM
0	1	+1XM
1	0	-1XM
1	1	0XM

Booth multiplier recoding table.



## Multiplication

- Considering 2's-complement signed operations, what will happen to  $(-13) \times (+11)$  if Sequential multiplication following the same method of unsigned multiplication?

Sign extension is shown in blue

					1	0	0	1	1	(-13)
					0	1	0	1	1	(+11)
					<hr/>					
	1	1	1	1	1	0	0	1	1	
	1	1	1	1	1	0	0	1	1	
	0	0	0	0	0	0	0	0		
	1	1	1	0	0	1	1			
	0	0	0	0	0					
	<hr/>									
	1	1	0	1	1	1	0	0	0	1 (-143)

Sign extension of negative multiplicand.

- $$\begin{array}{cccccccccccccccc}
 & & & & & & & & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\
 & & & & & & & & & & \hline 0 & 0 & +1 & +1 & +1 & +1 & & 0 \\
 & & & & & & & & & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 & & & & & & & & 0 & 1 & 0 & 1 & 1 & 0 & 1 & & \\
 & & & & & & 0 & 1 & 0 & 1 & 1 & 1 & 0 & 1 & & & \\
 & & & & 0 & 1 & 0 & 1 & 1 & 1 & 0 & 1 & & & & & \\
 & & & 0 & 1 & 0 & 1 & 1 & 1 & 0 & 1 & & & & & & \\
 & & 0 & 1 & 0 & 1 & 1 & 1 & 0 & 1 & & & & & & & \\
 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & & & & & & & & \\
 0 & 0 & 0 & 1 & 0 & 1 & 0 & 1 & 0 & 0 & 0 & 1 & 1 & 0
 \end{array}$$

- Since  $0011110 = 0100000 - 0000010$ , if we use the expression to the right, what will happen?

								0	1	0	1	1	0	1	
								0	+1	0	0	0	-1	0	
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	
1	1	1	1	1	1	1	1	0	1	0	0	1	1	←	2's complements of multiplicand
0	0	0	0	0	0	0	0	0	0	0	0	0			
0	0	0	0	0	0	0	0	0	0	0	0				
0	0	0	0	0	0	0	0	0	0	0					
0	0	0	1	0	1	1	0	1							
0	0	0	0	0	0	0	0								
0	0	0	1	0	1	0	1	0	0	0	1	1	0		

## Algorithm

- In general, in the Booth scheme,  $-1$  times the shifted multiplicand is selected when moving from 0 to 1, and  $+1$  times the shifted multiplicand is selected when moving from 1 to 0, as the multiplier is scanned from right to left.

0 0 1 0 1 1 0 0 1 1 1 0 1 0 1 1 0 0




0+1-1+1 0-1 0+1 0 0-1+1-1+1 0-1 0 0

Booth recoding of a multiplier.

THANK YOU
 
## Bit-Pair Recoding of Multipliers:

- Bit-pair recoding halves the maximum number of summands (versions of the multiplicand).



(a) Example of bit-pair recoding derived from Booth recoding

## Bit-Pair Recoding of Multipliers:

Multiplier bit-pair		Multiplier bit on the right $i_{-1}$	Multiplicand selected at position
$i+1$	$i$		
0	0	0	0 X M
0	0	1	+1 X M
0	1	0	+1 X M
0	1	1	+2 X M
1	0	0	-2 X M
1	0	1	-1 X M
1	1	0	-1 X M
1	1	1	0 X M

(b) Table of multiplicand selection decisions

Bit-Pair Recoding of Multipliers:

$$\begin{array}{r} 0\ 1\ 1\ 0\ 1\ (+13) \\ \times 1\ 1\ 0\ 1\ 0\ (-6) \\ \hline \end{array}$$



					0	1	1	0	1
					0	-1	+1	-1	0
					<hr/>				
0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	1	1	
0	0	0	0	1	1	0	1		
1	1	1	0	0	1	1			
0	0	0	0	0	0				
<hr/>					1	1	1	0	1
					1	0	0	1	0

(-78)



					0	1	1	0	1
					0		-1		-2
					<hr/>				
1	1	1	1	1	0	0	1	1	0
1	1	1	1	0	0	1	1		
0	0	0	0	0	0				
<hr/>					1	1	1	0	1
					1	0	0	1	0



THANK YOU